


Examples: Circuits

These are the images of the circuits from the pages in Set1 (Cedar Logic).

- Page 1 is implementation of NAND gate and NOT gate (from notes)
- Notation:
- p-type transistor has circle at gate
 - p-type closes when input to gate is 0
- n-type transistor does not have circle at gate
 - n-type closes when input to gate is 1


Set 1, Page 2: What is the function being implemented by this circuit ?

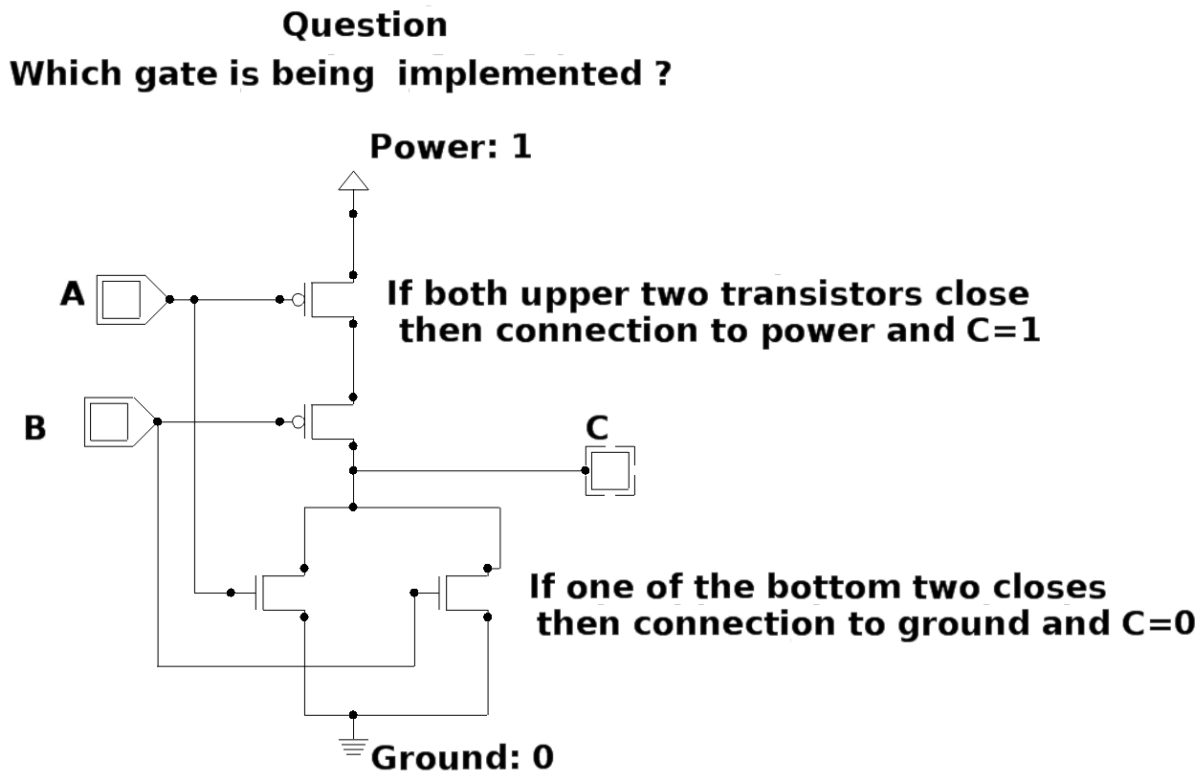- Inputs A, B and Output is C. Derive truth table



Set 1, Page 3: Combining 'gates'.

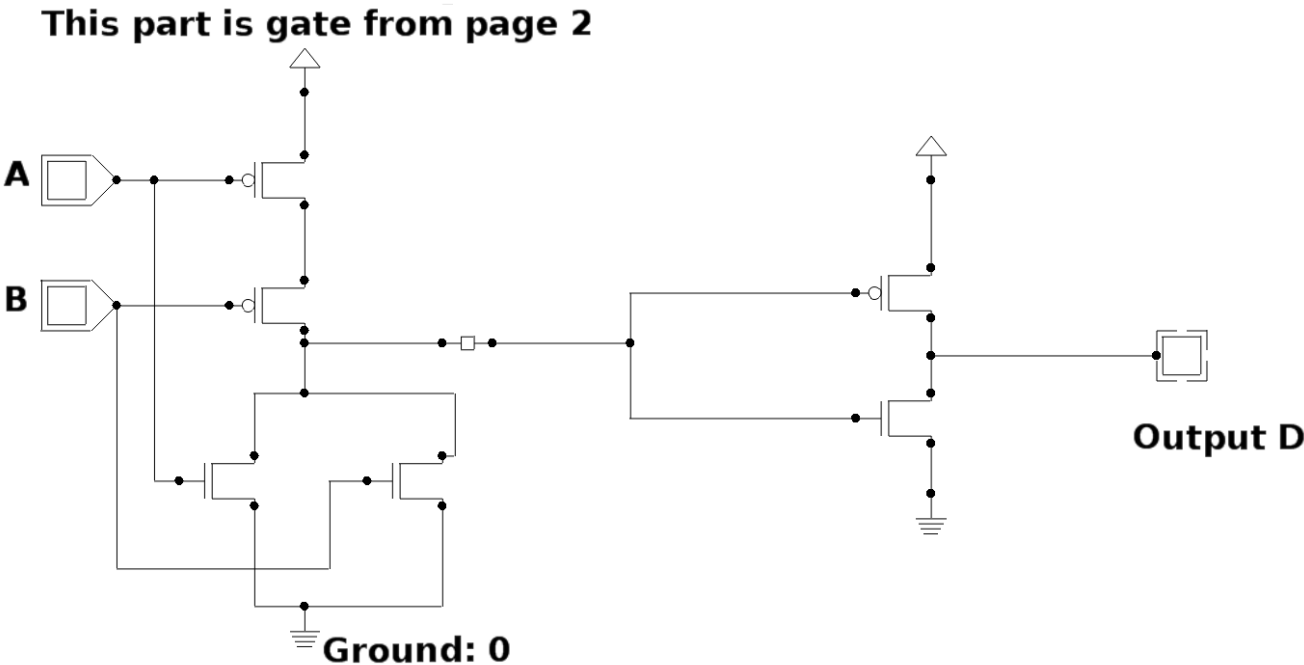
Which gate is being implemented?
Combining gates to build new 'gates'



Set 1, Page 4: Inputs A,B. Find truth table and function F

Find Truth Table for C,D,F


Ground: 0 \downarrow Power: 1 \uparrow

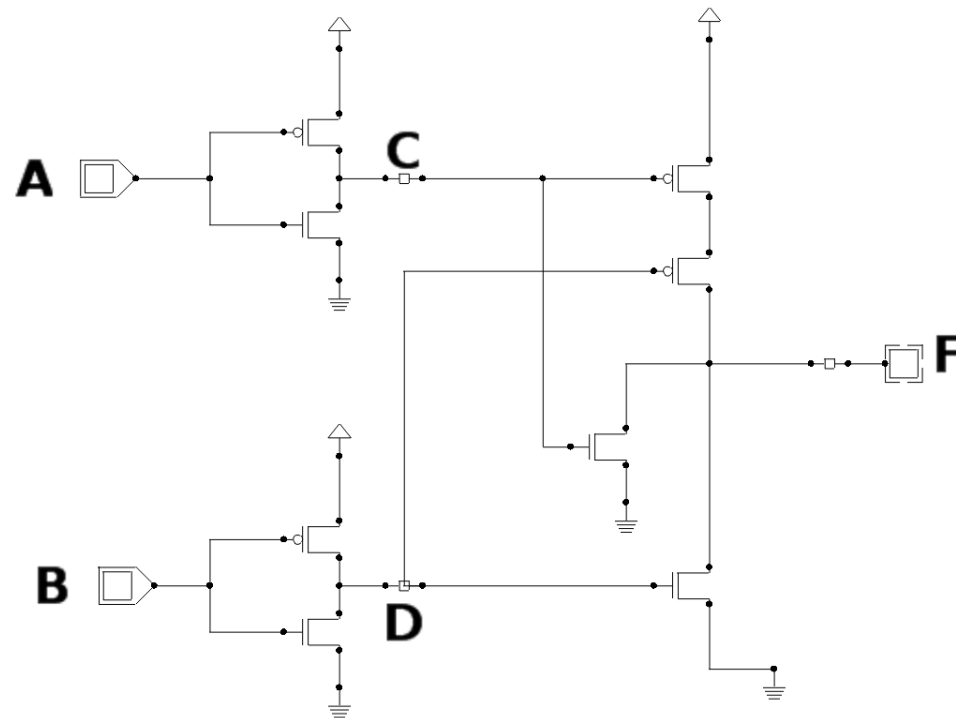


Set 1, Page 5: Examples of combinational circuits

Examples


A AND B

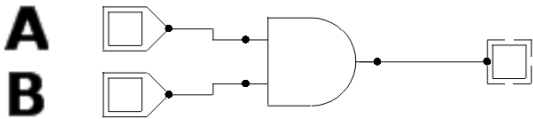

A OR B

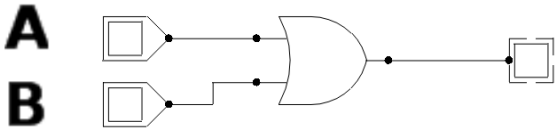


(A AND B) AND (NOT B OR C)

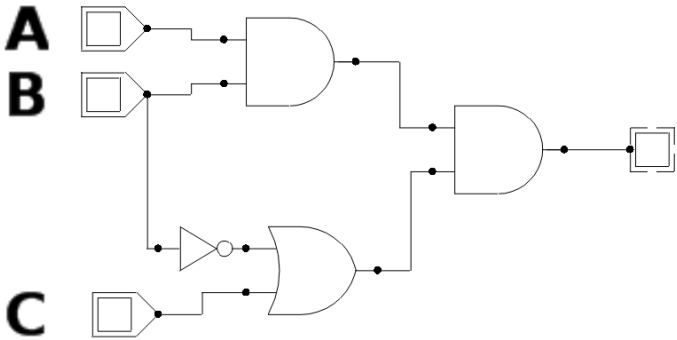

Set 1, Page 6

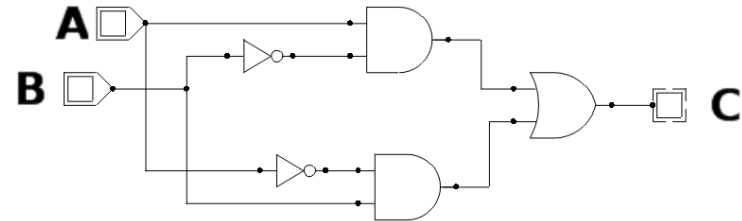(a) What is the boolean function for this circuit



(b) What is the boolean function F

